

# Digital Systems Design and Laboratory Final

2017-05-18

- Characteristic equations of flip-flops:
  - SR flip-flop:  $Q^+ = S + R'Q$
  - JK flip-flop:  $Q^+ = JQ' + K'Q$
  - D flip-flop:  $Q^+ = D$
  - T flip-flop:  $Q^+ = TQ' + T'Q = T \oplus Q$
- Moore and Mealy machine:
  - Constructed from truth tables to state tables and state diagrams.
  - **Regular expression** is generated for a desired output.

2017-05-25

- Reverse engineering
- State reduction:
  - Method of successive partitions.
  - Implication chart method.

2017-06-01

- Excitation table:

$Q$	$Q^+$	SR	JK	D	T
0	0	0-	0-	0	0
0	1	10	1-	1	1
1	0	01	-1	0	1
1	1	-0	-0	1	0

**2017-06-08**

- Six step process for forward design:
  - Understand the statement of the specification
  - Obtain an abstract specification of the FSM
  - Perform a state minimization
  - Perform state assignment
  - Choose FF types to implement FSM state register
  - Implement the FSM